

Tutorial 10: Fault Analysis


10.1 The one-line diagram for a power system is given in the following figure. The parameters of the generators and transformers are given as:

G1 and G2: 100MVA, 20kV, $X_1 = X_2 = 20\%$, $X_0 = 6\%$ and $X_N = 5\%$.

Transformers T₁ and T₂: 100MVA, 20Δ / 345Y kV and $X = 10\%$

Line (on bases 100MVA, 345kV): $X_1 = X_2 = 10\%$, $X_0 = 25\%$.

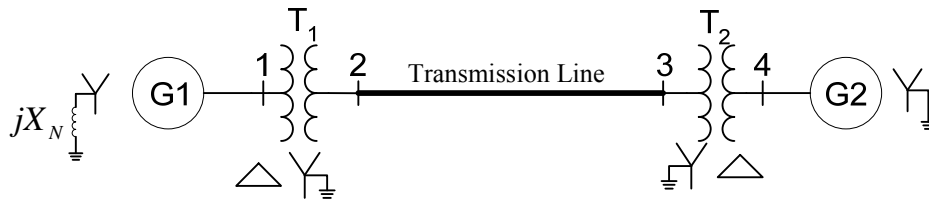
A bolted single line-to-ground fault occurs on phase *a* at bus 2. $V_f = 1 \angle 0^\circ$.




- Draw the sequence networks.
- Calculate the per unit sequence and phase currents at the fault point;
- Determine the per-unit phase currents flowing from Y side of T₁ to fault point;
- Determine the per-unit current flowing out of phase b of G1.

Solution:

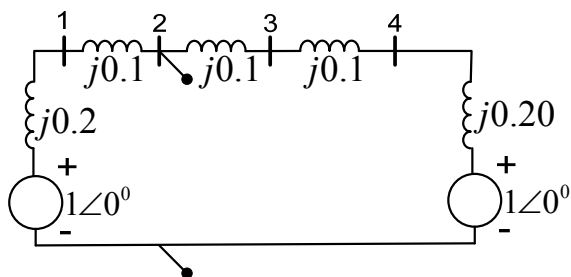
- a) Sequence networks: $Z_{th}^{(1)} = Z_{th}^{(2)} = j0.3 // j0.4 = j0.1714$, $Z_{th}^{(0)} = j0.35 // j0.1 = j0.0778$



(a) Positive-sequence network

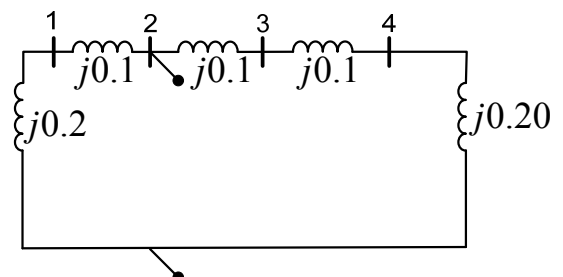


(b) Negative-sequence network

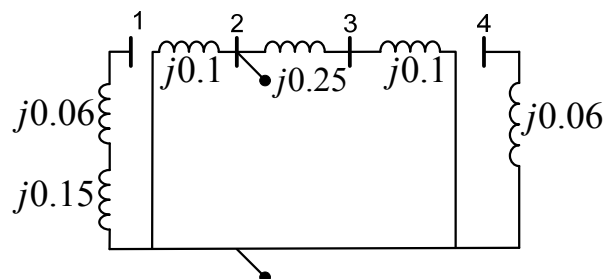

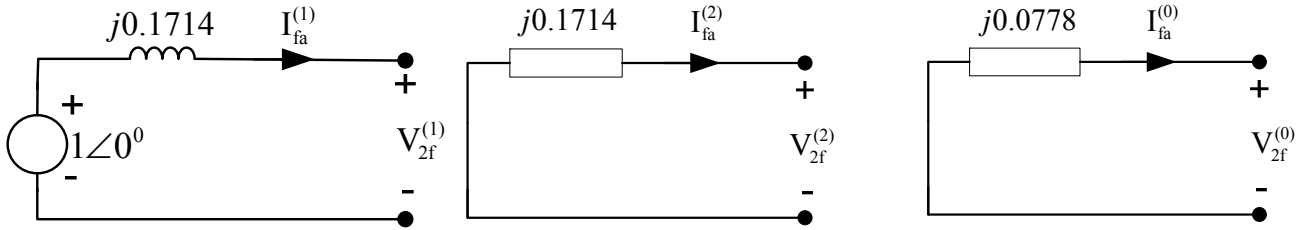(c) Zero-sequence network

The Thevenin equivalent circuits as viewed from bus 2:




b) Sequence networks connection:

The per unit sequence currents at the fault point:


$$I_{fa}^{(2)} = I_{fa}^{(1)} = I_{fa}^{(0)} = \frac{V_f}{Z_{th}^{(0)} + Z_{th}^{(1)} + Z_{th}^{(2)}} = 2.3776\angle -90^\circ$$

The per unit fault current at phase a :

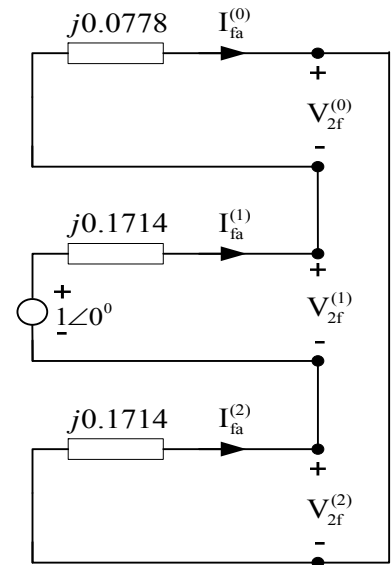
$$I_{fa} = I_{fa}^{(1)} + I_{fa}^{(2)} + I_{fa}^{(0)} = 3 \times 2.3776\angle -90^\circ = 7.1328\angle -90^\circ \text{ pu}$$



c) and d) The sequence networks:

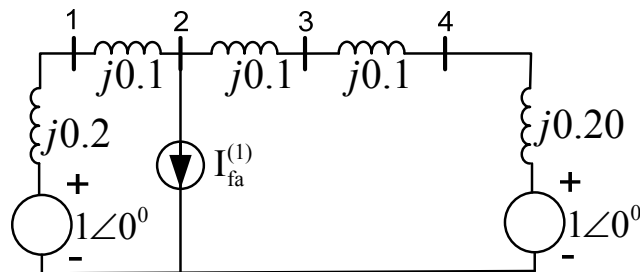


(a) Positive-sequence

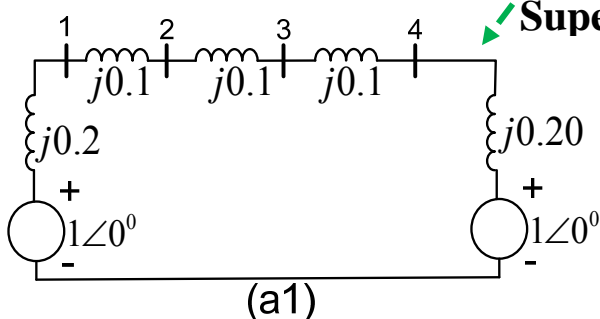

(a1)


Superposition

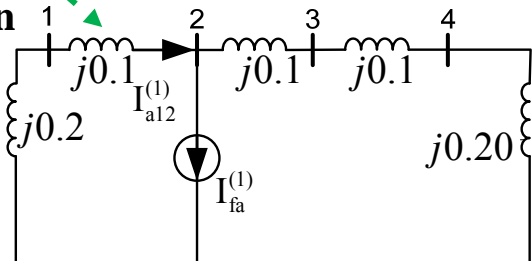


(a2)

The per unit positive sequence current flowing from T1 to fault bus 2:
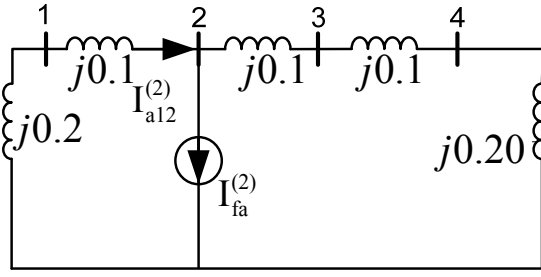
$$I_{a12}^{(1)} = \frac{j0.1 + j0.1 + j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times 2.3776\angle -90^\circ = 1.3586\angle -90^\circ \text{ pu}$$



(b) Negative-sequence

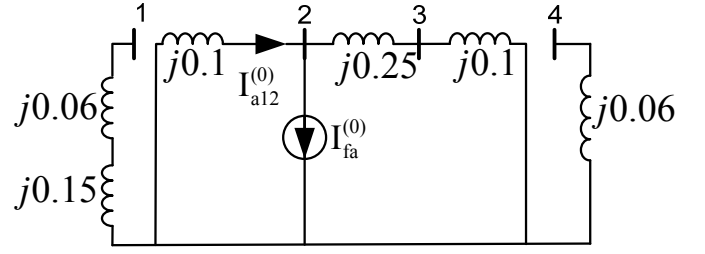

(c) Zero-sequence

The per unit negative sequence current flowing from T1 to fault bus 2:

$$I_{a12}^{(2)} = \frac{j0.1 + j0.1 + j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times 2.3776 \angle -90^\circ = 1.3586 \angle -90^\circ \text{ pu}$$

The per unit zero sequence current flowing from T1 to fault bus 2:

$$I_{a12}^{(0)} = \frac{j0.25 + j0.1}{(j0.25 + j0.1) + j0.1} \times 2.3776 \angle -90^\circ = 1.8492 \angle -90^\circ \text{ pu}$$

The per unit fault currents flowing from T1 to fault Bus 2:

$$\begin{bmatrix} I_{a12} \\ I_{b12} \\ I_{c12} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a12}^{(0)} \\ I_{a12}^{(1)} \\ I_{a12}^{(2)} \end{bmatrix} = [\mathbf{A}] \begin{bmatrix} 1.8492 \angle -90^\circ \\ 1.3586 \angle -90^\circ \\ 1.3586 \angle -90^\circ \end{bmatrix} = \begin{bmatrix} 4.5664 \angle -90^\circ \\ 0.4906 \angle -90^\circ \\ 0.4906 \angle -90^\circ \end{bmatrix} \text{ pu}$$

e) The per unit sequence currents of phase a out of G1:

$$I_{a,G1}^{(0)} = 0$$

$$I_{a,G1}^{(1)} = I_{a12}^{(1)} \times 1 \angle -30^\circ = 1.3586 \angle (-90^\circ - 30^\circ) = 1.3586 \angle -120^\circ$$

$$I_{a,G1}^{(2)} = I_{a12}^{(2)} \times 1 \angle 30^\circ = 1.3586 \angle (-90^\circ + 30^\circ) = 1.3586 \angle -60^\circ$$

The per unit fault current out of Phase b of G1:


$$\begin{aligned} I_{b,G1} &= I_{a,G1}^{(0)} + a^2 I_{a,G1}^{(1)} + a I_{a,G1}^{(2)} = 1.3586 \angle 120^\circ + 1.3586 \angle 60^\circ \\ &= 2.3532 \angle 90^\circ \text{ pu} \end{aligned}$$

10.2 A bolted double line-to-ground fault between phase b and c occurs at bus 2 in the power system shown in question 5.1.

- Calculate the per unit sequence currents at the fault point;
- Calculate the per unit phase voltages at bus 3.

Solution:

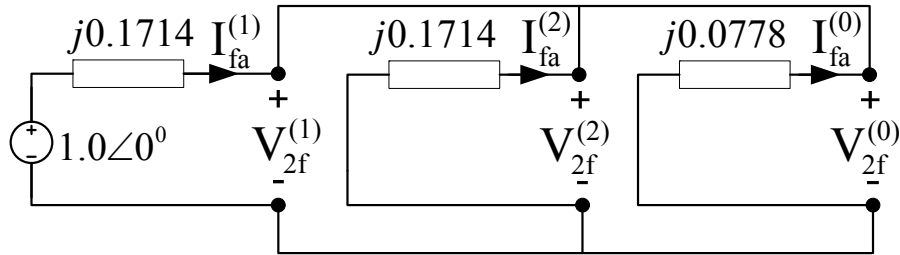
- Sequence currents at the fault location:



$$I_{fa}^{(1)} = \frac{V_f}{Z_{th}^{(1)} + Z_{th}^{(2)} // Z_{th}^{(0)}} = -j4.4462, \quad I_{fa}^{(2)} = -I_{fa}^{(1)} \frac{Z_{th}^{(0)}}{Z_{th}^{(0)} + Z_{th}^{(2)}} = j1.3881$$

$$I_{fa}^{(0)} = -I_{fa}^{(1)} \frac{Z_{th}^{(2)}}{Z_{th}^{(0)} + Z_{th}^{(2)}} = j3.0581$$

- The phase-to-ground voltages at bus 3:

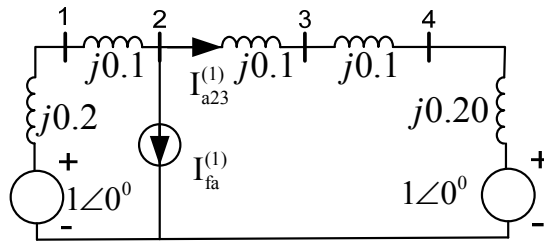


(a) Positive-sequence

The positive sequence current flowing from bus 2 to bus 3:

$$I_{a23}^{(1)} = -\frac{j0.1 + j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times (-j4.4462) = j1.9055 \text{ pu}$$

The positive sequence voltages at bus 3:
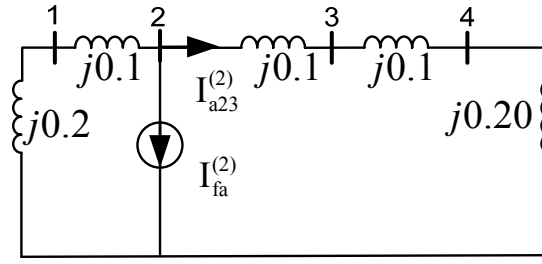
$$V_3^{(1)} = 1.0\angle 0^\circ + (j0.1 + j0.2) \times I_{a23}^{(1)} = 1.0\angle 0^\circ + j0.3 \times j1.9055 = 0.4284 \text{ pu}$$




(b) Negative-sequence

The negative sequence current flowing from bus 2 to bus 3:

$$I_{a23}^{(2)} = -\frac{j0.1 + j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times j1.3881 = -j0.5949 \text{ pu}$$

The negative sequence voltages at bus 3:
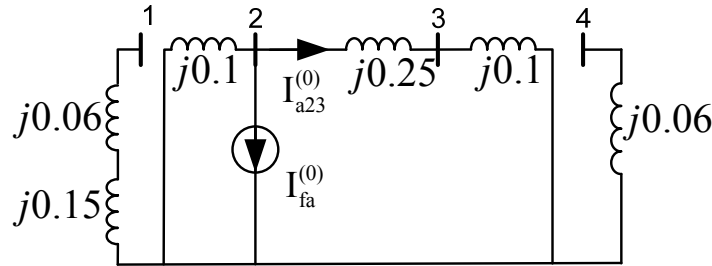
$$V_3^{(2)} = (j0.1 + j0.2) \times I_{a23}^{(2)} = j0.3 \times (-j0.5949) = 0.1785 \text{ pu}$$



(c) Zero-sequence

The zero sequence current flowing from bus 2 to bus 3:

$$I_{a23}^{(0)} = -\frac{j0.1}{(j0.25 + j0.1) + j0.1} \times j3.0581 = -j0.6796 \text{ pu}$$

The zero sequence voltages at bus 3:

$$V_3^{(0)} = j0.1 \times (-j0.6796) = 0.0680 \text{ pu}$$


The phase voltages at bus 3:

$$\begin{bmatrix} V_{3a} \\ V_{3b} \\ V_{3c} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_3^{(0)} \\ V_3^{(1)} \\ V_3^{(2)} \end{bmatrix} = \begin{bmatrix} 0.6749 \\ 0.3198 \angle -137.4^\circ \\ 0.3198 \angle 137.4^\circ \end{bmatrix} \text{ p.u.}$$


10.3 A double line fault between phase b and c with the fault impedance $X_f=0.1\text{pu}$ occurs at bus 1 in the power system shown in question 10.1.

- Calculate the per unit sequence currents through transmission line. (Students: calculate phase currents from the sequence currents)
- Calculate the sequence voltages at bus 3. (Students: calculate phase voltages from the sequence voltages)

Solution:

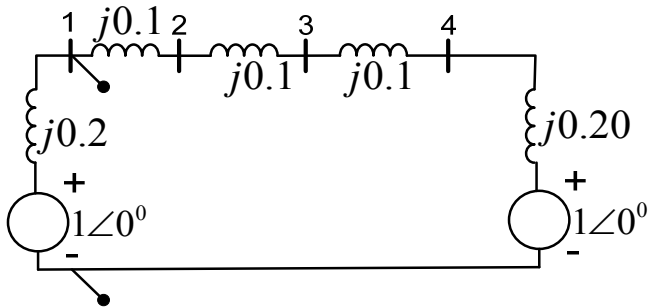

(a) Positive-sequence network

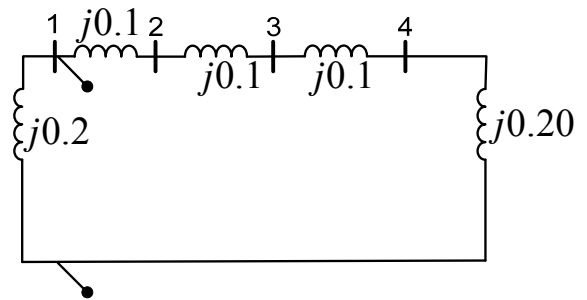


(b) Negative-sequence network

Thevenin positive and negative, equivalent impedances viewed from bus 1: $Z_{th}^{(2)} = Z_{th}^{(1)} = j0.2 // j0.5 = j0.14286$


Sequence currents:
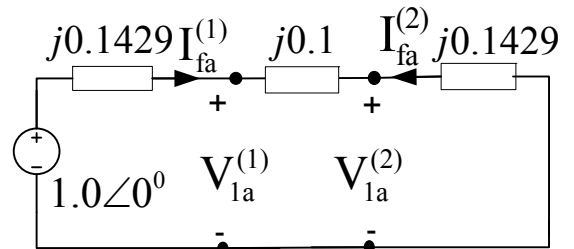
$$I_{fa}^{(1)} = -I_{fa}^{(2)} = \frac{V_f}{Z_{th}^{(1)} + Z_{th}^{(2)} + Z_f} = -j2.592$$




Sequence networks connection

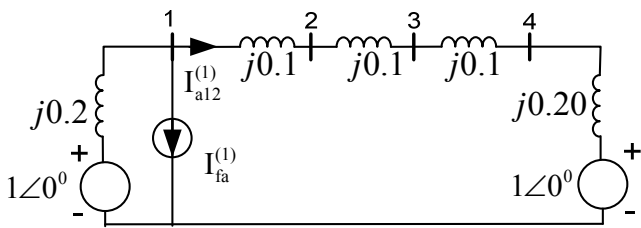a) The phase current through transmission line:



(a) Positive-sequence

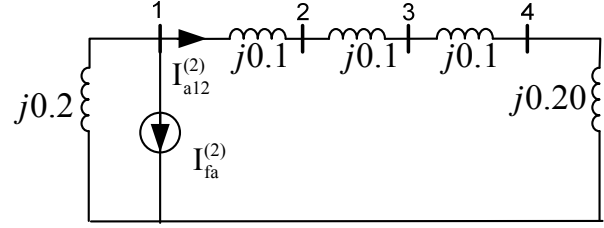

(a) Negative-sequence

Sequence currents from bus 1 to Δ side of T1:

$$I_{a12}^{(1)} = -\frac{j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times (-j2.592) = j0.741 \text{ pu}$$

$$I_{a12}^{(2)} = -\frac{j0.2}{(j0.1 + j0.1 + j0.2) + (j0.1 + j0.2)} \times (j2.592) = -j0.741 \text{ pu}$$

$$I_{a12}^{(0)} = 0$$

Sequence currents from bus 2 to 3 (Y side of T1):

$$I_{a23}^{(1)} = I_{a12}^{(1)} \angle 30^\circ = 0.741 \angle 120^\circ \text{ pu} = -0.3705 + j0.6417 \text{ pu}$$


$$I_{a23}^{(2)} = I_{a12}^{(2)} \angle -30^\circ = 0.741 \angle -120^\circ \text{ pu} = -0.3705 - j0.6417 \text{ pu}$$

$$I_{a23}^{(0)} = 0$$


Phase currents through line:

$$\begin{bmatrix} I_{a23} \\ I_{b23} \\ I_{c23} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a23}^{(0)} \\ I_{a23}^{(1)} \\ I_{a23}^{(2)} \end{bmatrix} = \begin{bmatrix} ? \\ ? \\ ? \end{bmatrix} \text{ p.u.}$$

b) The phase voltages at bus 3

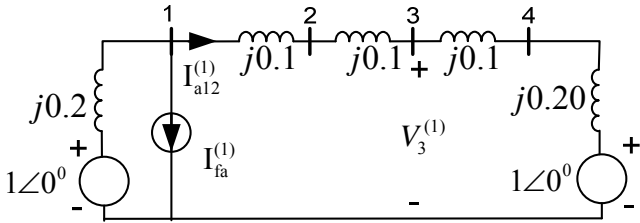

(a) Positive-sequence

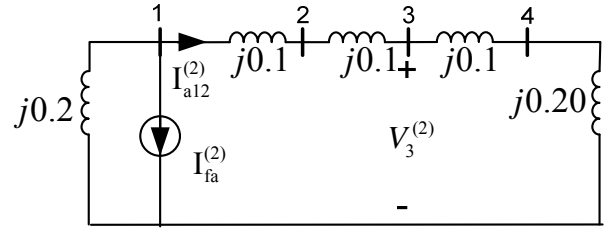

(a) Negative-sequence

The sequence voltages at bus 3 without considering current phase shift:

$$V_3^{(1)} = 1.0 \angle 0^\circ + (j0.1 + j0.2) \times I_{a12}^{(1)} = ? \text{ pu}$$

$$V_3^{(2)} = (j0.1 + j0.2) \times I_{a12}^{(2)} = ? \text{ pu}$$

$$V_3^{(0)} = 0 \text{ pu}$$

The phase voltages at bus 3 after considering phase shift (bus 3 is on Y side of T1):

$$\begin{bmatrix} V_{3a} \\ V_{3b} \\ V_{3c} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_3^{(0)} \\ V_3^{(1)} \angle 30^\circ \\ V_3^{(2)} \angle -30^\circ \end{bmatrix} = \begin{bmatrix} ? \\ ? \\ ? \end{bmatrix} \text{ p.u.}$$